
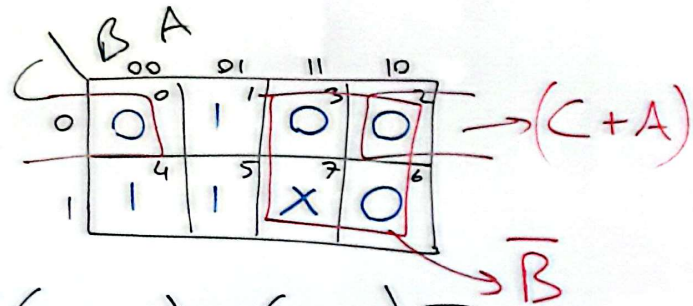


$$F(C, B, A) = \prod M(0, 2, 3, 6) \cdot \prod (7)$$

a) En sade halini bulunuz. (40 puan)


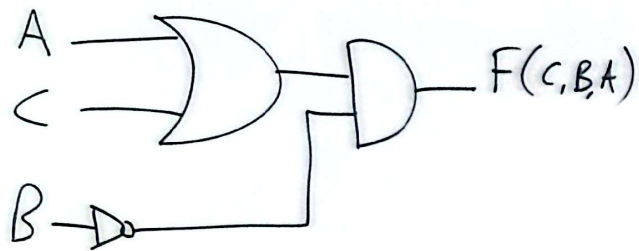


$$F(C, B, A) = (C + A) \cdot \bar{B}$$




b) 4x1 Max ile devreyi tasarlayınız ($S_1 = C, S_0 = B$) (25 puan)

C	B	A=0	A=1
S_1	S_0		
0	0	0	1
0	1	0	0
1	0	1	1
1	1	0	X

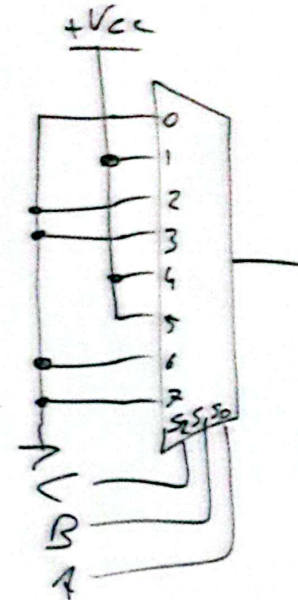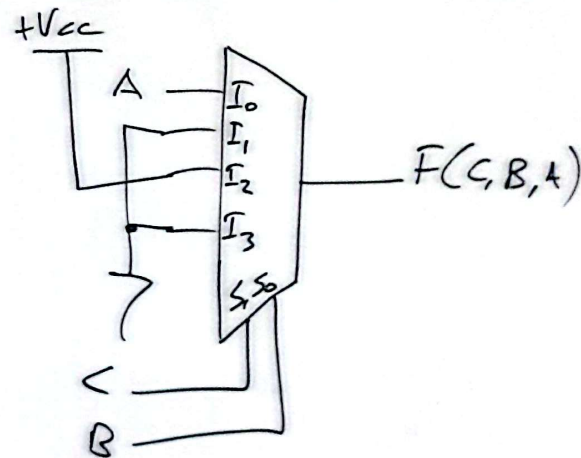

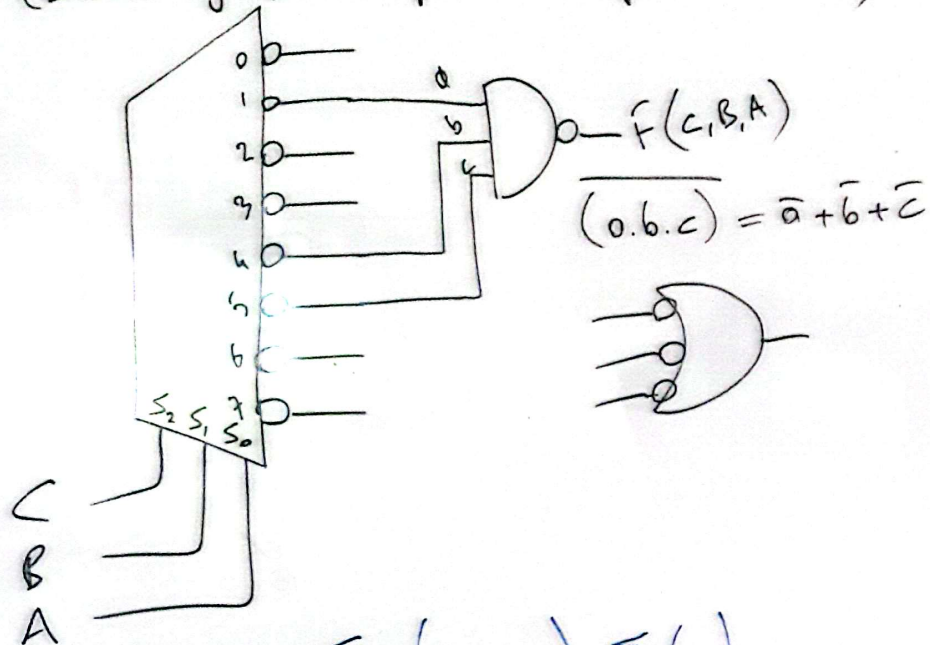3) 3x8 dekodör ile devreyi tasarlayınız.
(En az girişe sahip temel kapı kullanarak) (25 puan)



$$F(C,B,A) = \sum m(\underline{1,4,5}) + \sum (7)$$

