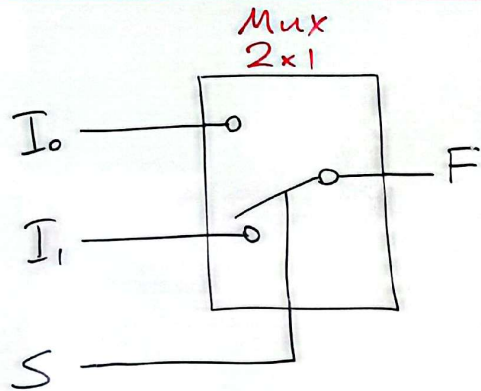


Mux (Multiplexers) - Veri Çoklayıcılar




$$S=0 \Rightarrow F=I_0$$

$$S=1 \Rightarrow F=I_1$$

S	I ₁	I ₀	F	
0	0	0	0	
0	0	1	1	$\rightarrow \bar{S} \cdot \bar{I}_1 \cdot I_0$
0	1	0	0	
0	1	1	1	$\rightarrow \bar{S} \cdot I_1 \cdot I_0$
1	0	0	0	
1	0	1	0	
1	1	0	1	$\rightarrow S \cdot I_1 \cdot \bar{I}_0$
1	1	1	1	$\rightarrow S \cdot I_1 \cdot I_0$

$\bar{S} \cdot \bar{I}_1 \cdot I_0 + \bar{S} \cdot I_1 \cdot I_0 = \bar{S} \cdot I_0$
 $S \cdot I_1 \cdot \bar{I}_0 + S \cdot I_1 \cdot I_0 = S \cdot I_1$
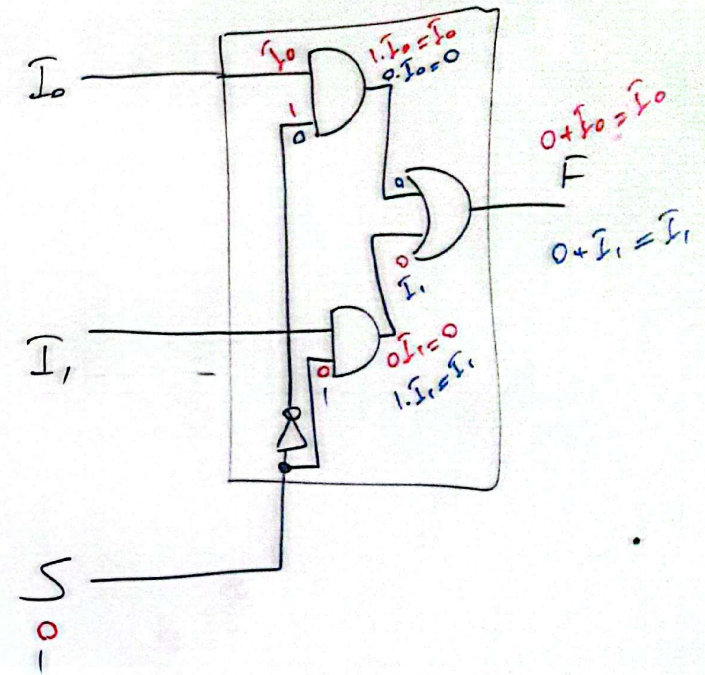
$$F(S, I_1, I_0) = \bar{S} \cdot I_0 + S \cdot I_1$$





$$F(C, B, A) = \sum (2, 4, 5, 6)$$

a) 8x1 Mux ile devreyi tasarlayınız.

b) 4x1 " " " " (S₁=B, S₀=A)

c) 2x1 " " " " (S₀=C)

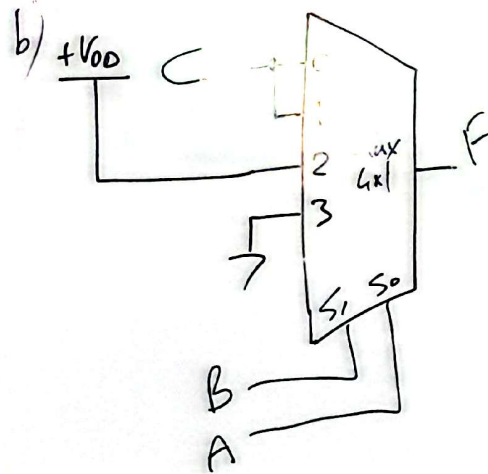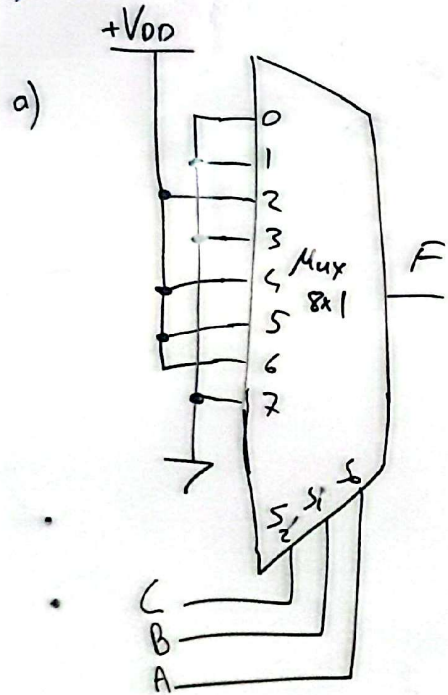

	C	B	A	F
0 →	0	0	0	0
1 →	0	0	1	0
2 →	0	1	0	1
3 →	0	1	1	0
0 →	1	0	0	1
1 →	1	0	1	1
2 →	1	1	0	1
3 →	1	1	1	0

c)

C	B	A	F
0	0	0	0
0	0	1	0
0	1	0	1 → B· $\bar{A}$
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0 → $\bar{B} + \bar{A}$

