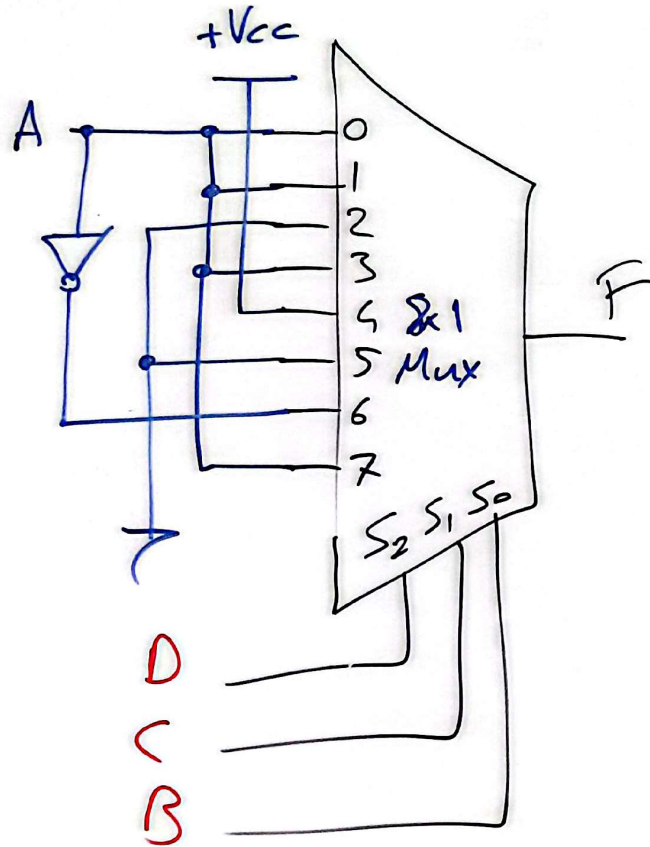


Örnek: $F(D, C, B, A) = \sum m(1, 3, 7, 8, 12, 15) + \sum d(4, 6, 9)$

a) 8×1 Mux ($S_2 = D, S_1 = C, S_0 = B$)


b) 4×1 Mux ($S_1 = A, S_0 = B$)

a)



	S_2	S_1	S_0		
	D	C	B	A=0	A=1
0	0	0	0	0	1
1	0	0	1	0	1
2	0	1	0	X=0	0
3	0	1	1	X=0	1
4	1	0	0	1	X=1
5	1	0	1	0	0
6	1	1	0	1	0
7	1	1	1	0	1

b)

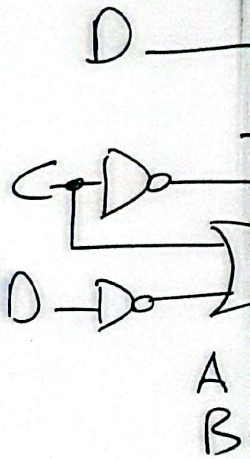


$$F(C, B, A) = \sum_m(1, 3, 4, 7) + \sum_d(2)$$

- a) 4x1 Mux ($S_1 = C, S_0 = A$)
- b) 2x1 Mux ($S = B$)

a)

	S_1	S_0	$B=0$	$B=1$
I_0	C	A		
I_1	0	0	0 ⁰	1 ² → 0
I_2	0	1	1 ¹	1 ³ → 1
I_3	1	0	1 ⁴	0 ⁶ → $\overline{B}$
I_4	1	1	0 ⁵	1 ⁷ → B

d: Don't Care

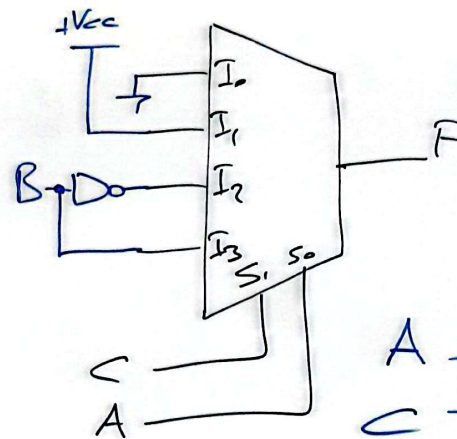

b)

S	$C=0$ $A=0$	$C=0$ $A=1$	$C=1$ $A=0$	$C=1$ $A=1$
I_0	0 ⁰	1 ¹	1 ⁴	0 ⁵
I_1	1 ²	1 ³	0 ⁶	1 ⁷

→ $A \oplus C$
→ A

