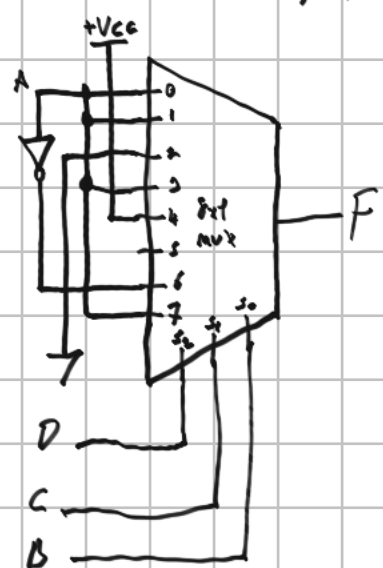
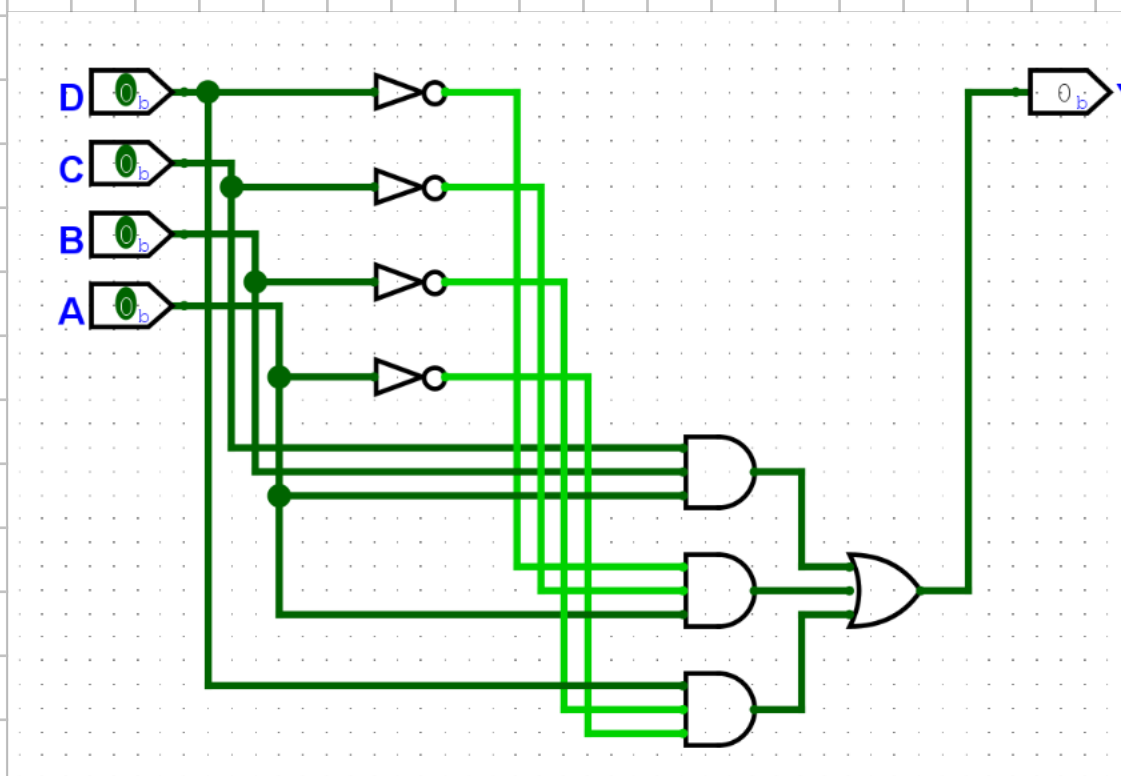


Örnek: $F(D, C, B, A) = \sum m(1, 3, 7, 8, 12, 13) + \sum d(4, 6, 9)$



8x1 mux
($S_2 = D, S_1 = C, S_0 = B$)

	S_2	S_1	S_0				
	D	C	B	A=1	A=0		
0	0	0	0	0	1	1	A
1	0	0	1	0	1	3	A
2	0	1	0	X=0	0	5	0
3	0	1	1	X=0	1	7	A
4	1	0	0	1	X=1	9	1
5	1	0	1	0	0	11	0
6	1	1	0	1	0	13	$\bar{A}$
7	1	1	1	0	1	15	A



4x1 mux ile ($S_1 = A, S_0 = B$)

	S_1	S_0					
	A	B	C=0 D=0	C=0 D=1	C=1 D=0	C=1 D=1	
I_0	0	0	0	1	X=0	1	$\rightarrow D$
I_1	0	1	0	0	X=0	0	$\rightarrow 0$
I_2	1	0	1	X=1	0	0	$\rightarrow \bar{C}$
I_3	1	1	1	0	1	1	$\rightarrow C + \bar{D}$

C \ D	0	1
0	1	0 $\rightarrow C + \bar{D}$
1	1	1

